



**AMRITA**  
VISHWA VIDYAPEETHAM

**Course Code:** 19ECE383

**Course Name:** VLSI Design Lab

**Component:** System Design

**Semester/Section:** VI/C

**Date of Evaluation:** 29-04-2025

**Academic Year:** 2024-2025 (Even Semester)

**Batch Number for System Design:** 8

**Name of the Students:** 1) K Pallavi ECE22224

**With Registration no.** 2) K Mahesh ECE22227

3) M L Shrividya ECE22228

**Branch:** Electronics and Communication Engineering

**Semester, Section, Batch:** VI,C,C1

**Batch:** 2022-2026

**Faculty In-charge:** Ms. Sonali Agrawal

**Aim1:**

To design and implement a 2-bit ALU capable of performing:


- 2-bit Addition
- 2-bit Subtraction using full adders and required logic gates
- 2-input XOR using Mirror circuit
- 2-input AND using minimum number of Transmission gates using Cadence Virtuoso with 45nm Technology.

**Tool Used:** Cadence Virtuoso

**Technology Used:** 45nm CMOS Technology

**Theory:****1) Introduction**

An Arithmetic Logic Unit (ALU) is a critical component of a processor, performing arithmetic and logic operations. In this experiment, a 2-bit ALU is designed to perform addition, subtraction, XOR, and AND operations. Control logic selects the desired operation based on input signals.

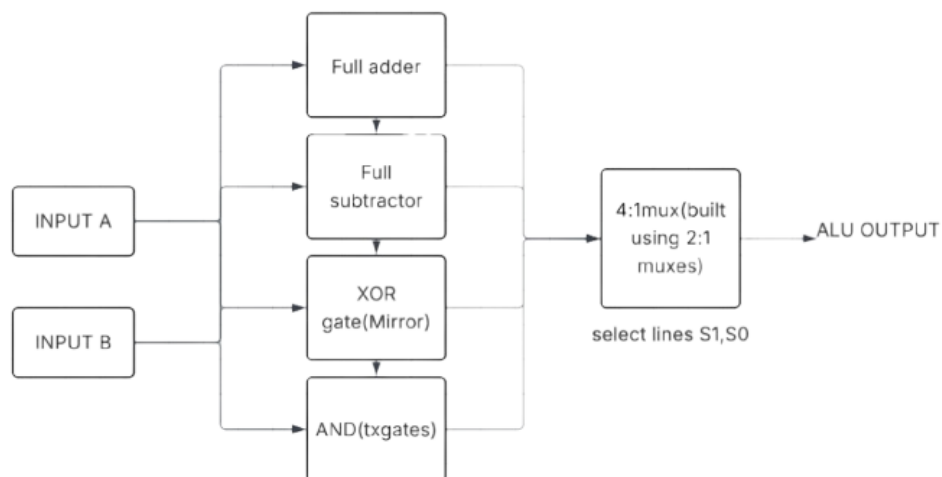**2) Block Diagram of the designed ALU with working principle**


Inputs A and B are simultaneously fed to four blocks: a full adder, full subtractor, XOR gate, and AND gate. The full adder produces the sum of A and B, the full subtractor gives the difference (A - B), the XOR gate performs the bitwise XOR of A and B, and the AND gate performs the bitwise AND of A and B. The outputs from these four blocks are then given as inputs to a 4:1 multiplexer. Based on the select lines (S1, S0), the multiplexer selects one of these operations' results to pass to the ALU output.

S1	S0	Operation Selected	ALU Output
0	0	Full Adder	$A + B$
0	1	Full Subtractor	$A - B$
1	0	XOR Gate (Mirror)	$A \oplus B$
1	1	AND Gate (Txgates)	$A \cdot B$ (A AND B)
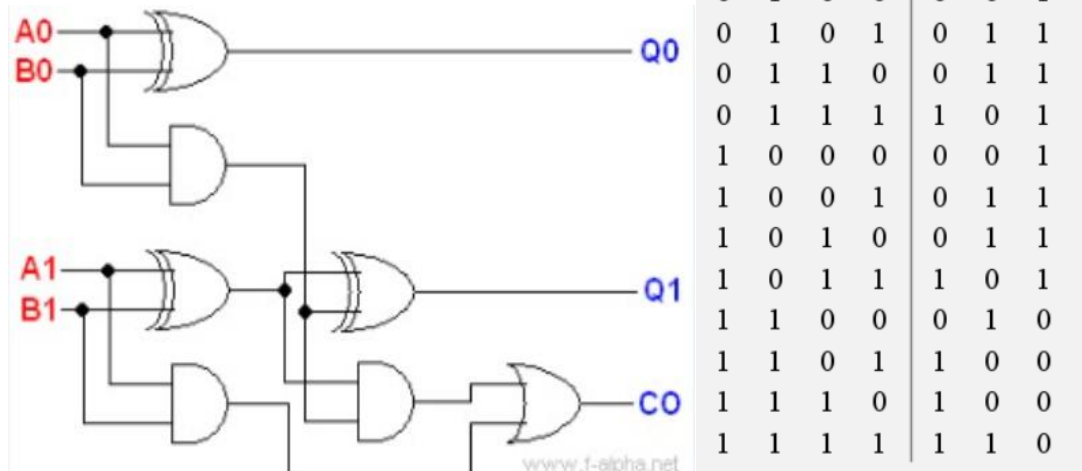
### 3) Logic Circuit for each block of ALU with working principle (including Truth Table and Logical expressions)


- **2-bit Addition:**

Implemented using full adders cascading carry-out to next stage.


 
#### Logical expressions


- $S0 = A0 \oplus B0$
  - $C0 = A0 \cdot B0$
  - $S1 = A1 \oplus B1 \oplus C0$
  - $C1 = (A1 \cdot B1) + (B1 \cdot C0) + (A1 \cdot C0)$
- **2-bit Subtraction:**  
Built using full adders and logic inversion (2's complement method).



Input					Output		
V(const)	V(d)	V(c)	V(b)	V(a)	Carry	Sum1	Sum0
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	1
0	0	0	1	0	0	0	1
0	0	0	1	1	0	1	0
0	0	1	0	0	0	1	0
0	0	1	0	1	0	1	1
0	0	1	1	0	0	1	1
0	0	1	1	1	1	0	0
0	1	0	0	0	0	1	0
0	1	0	0	1	0	1	1
0	1	0	1	0	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	0	1	0	0
0	1	1	0	1	1	0	1
0	1	1	1	0	1	0	1
0	1	1	1	1	1	1	0
1	0	0	0	0	1	0	0
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1
1	0	0	1	1	1	0	0
1	0	1	0	0	0	1	0
1	0	1	0	1	0	0	1
1	0	1	1	0	0	1	1
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	0
1	1	0	0	1	1	0	1
1	1	0	1	0	1	1	1
1	1	0	1	1	1	1	0
1	1	1	0	0	1	0	0
1	1	1	0	1	0	1	1
1	1	1	1	0	1	0	1
1	1	1	1	1	1	0	0
 
### Logical expressions

- $D0 = A0 \oplus B0$
  - $B0 = (\sim A0) \cdot B0$
  - $D1 = A1 \oplus B1 \oplus B0$
  - $B1 = (\sim A1) \cdot (B1 + B0) + (B1 \cdot B0)$
- **2-input XOR using Mirror Circuit:**  
Designed with a symmetrical (mirror) layout for reduced delay and power.




A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0
 
### Logical expression

$$Y = (A \cdot \sim B) + (\sim A \cdot B)$$

- **2-input AND using minimum number of Transmission Gates:**  
Efficient design for minimal area and power.



A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

Logical expression


$$A \cdot B$$

## CMOS Schematics


Design Specifications:

Supply Voltage	1V
Transistor Length	45 nm
Transistor Width	120 nm
Input Signal Frequency	Upto 1GHz

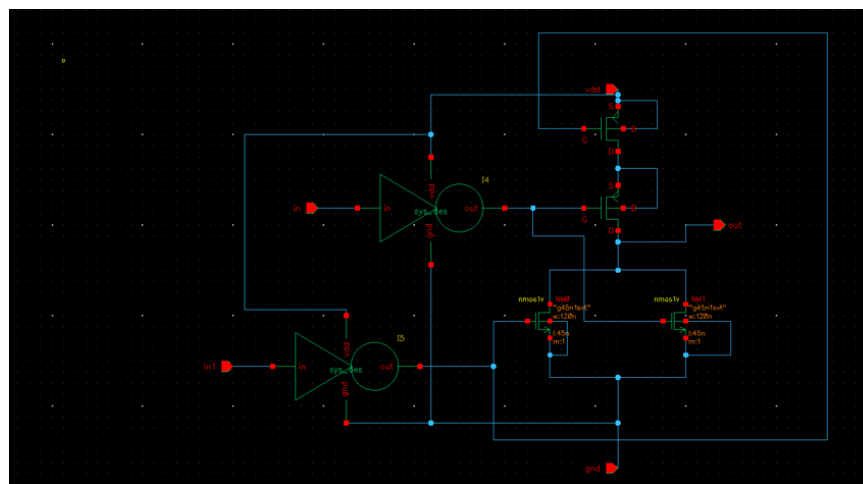
Schematic Screenshots from the tool (Each block of ALU + Complete ALU Design):




AND Gate

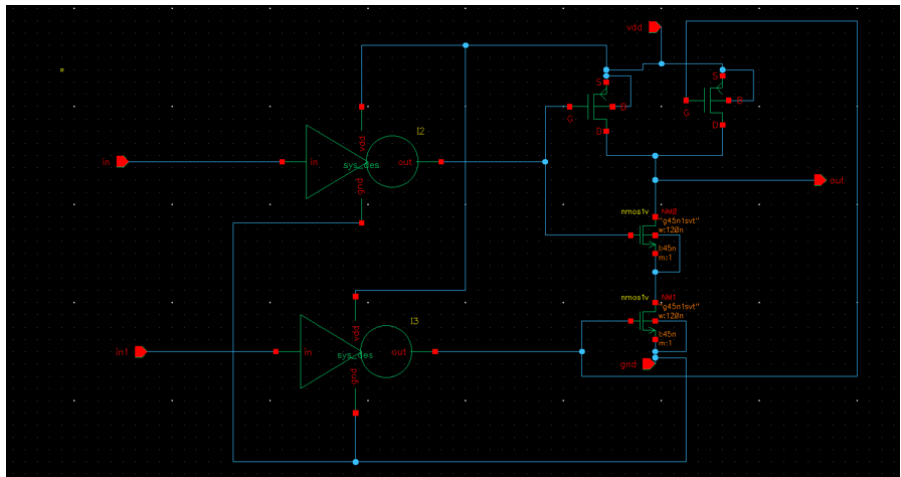


OR Gate

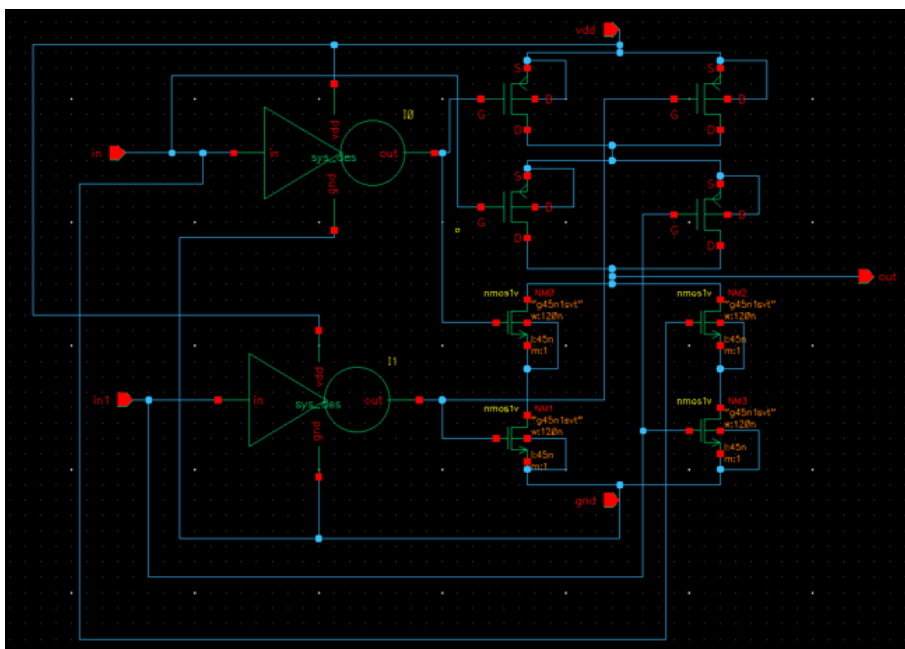


XOR Gate

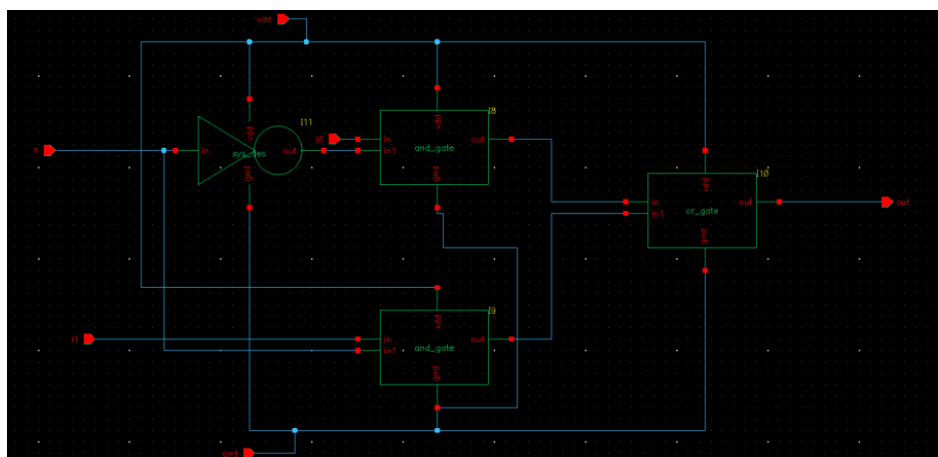


2:1 MUX

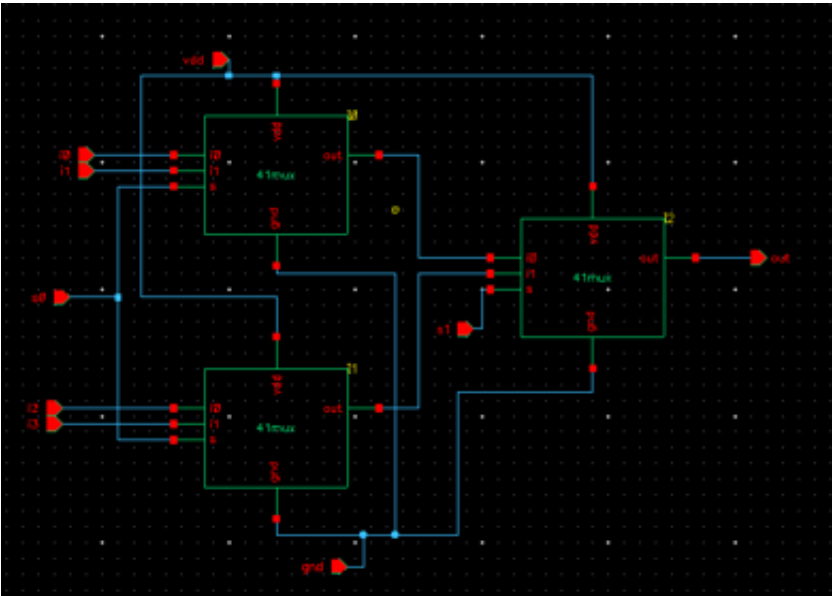


4:1MUX

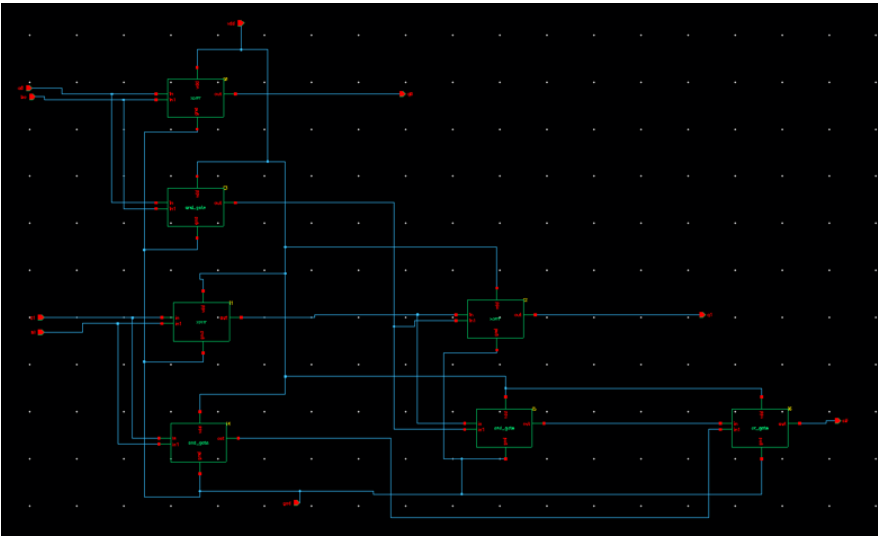


2 bit addition

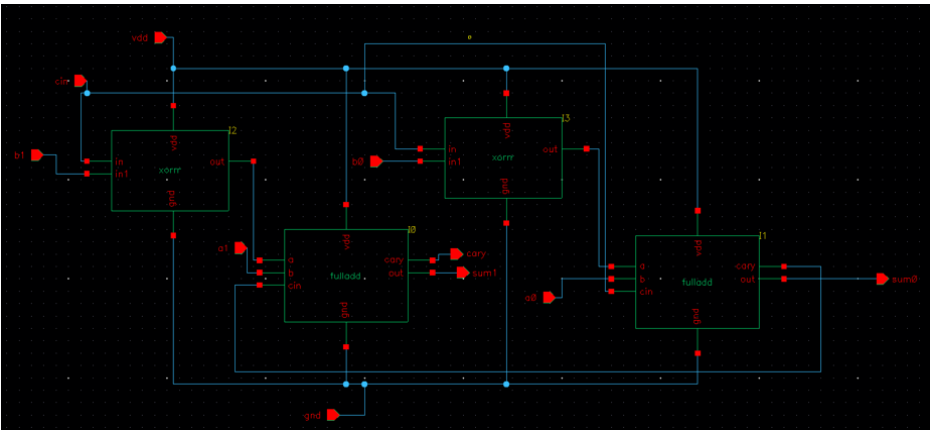


2 bit subtractor

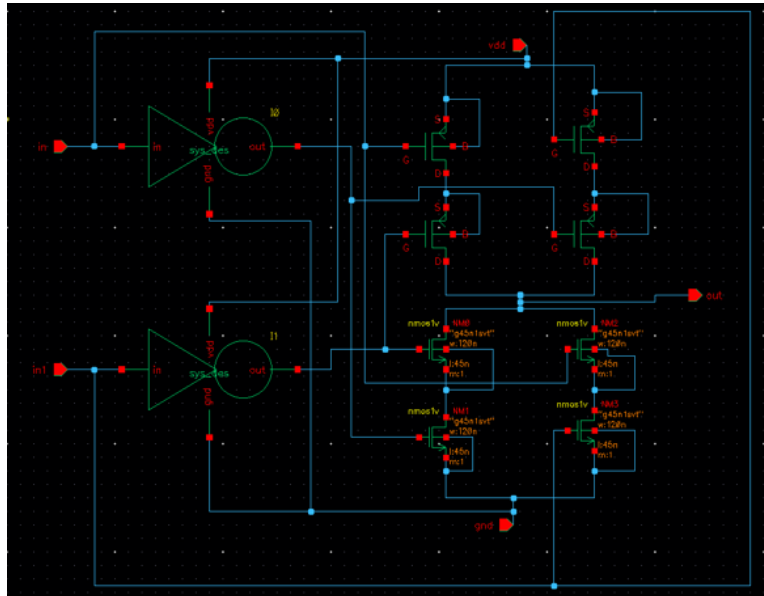

2-input XOR using Mirror circuit

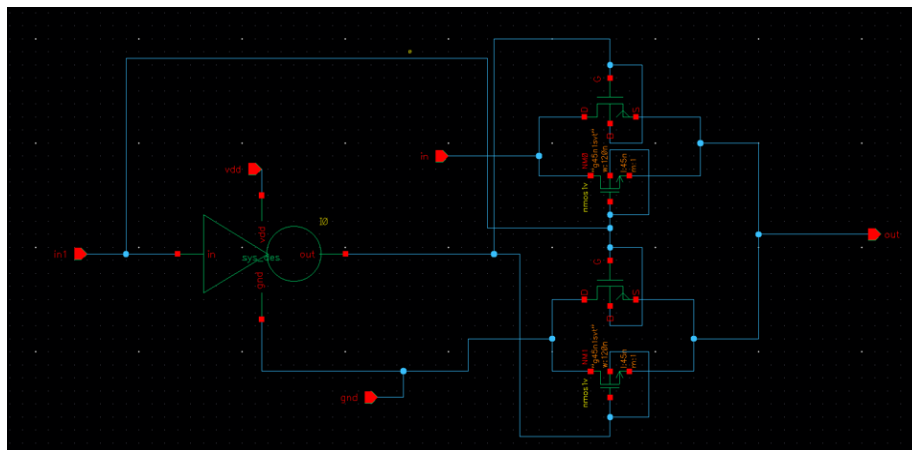

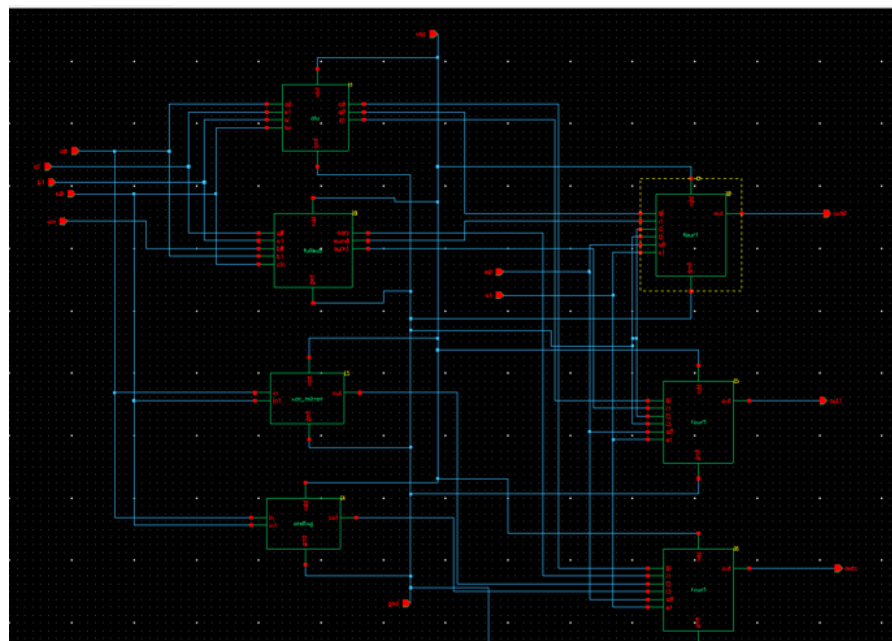
2-input AND using minimum number of Transmission gates




Complete ALU Design



 
## Simulation Results (Screenshot from the tool-Each block of ALU + Complete ALU Design):




2-bit Addition

 

 2-bit Subtraction using full adders and required logic gates



2-input XOR using Mirror circuit

 

2-input AND using minimum number of Transmission gates

## Conclusion:

The ALU was successfully designed and implemented using Cadence Virtuoso at 45nm technology node. All operations (Addition, Subtraction, XOR, AND) were verified through schematic design and simulation. The use of mirror circuits and transmission gates resulted in optimized performance in terms of area and power.

## Aim 2:

To design and implement a 4-bit ALU capable of performing :

- 4-bit Addition
- 4-bit Subtraction using full adders and required logic gates
- 4-bit Left shift SISO shift register
- 4-bit Ring Counter

**Tool Used:** Xilinx Vivado 2024.2


**FPGA Family (for Synthesis):** Virtex-7

## Theory:

### 1) Introduction

This Verilog module implements a simple 4-bit Arithmetic Logic Unit (ALU) that performs fundamental arithmetic and logic operations based on a 2-bit control signal. Operating synchronously with a clock input (clk), it accepts two 4-bit inputs (A and B) and outputs a 4-bit result along with a carry-out flag and a zero flag. The ALU supports four operations: addition (control = 00), subtraction (control = 01), a serial-in serial-out (SISO) left shift (control = 10), and a ring counter operation (control = 11). In addition and subtraction modes, it calculates the result and sets the carry and zero flags accordingly. In shift mode, it loads and shifts A left over successive clock cycles. The ring counter rotates the bits of A left by one position, effectively forming a circular shift. This ALU is suitable for basic computational tasks in digital systems and can be integrated into larger sequential logic designs.

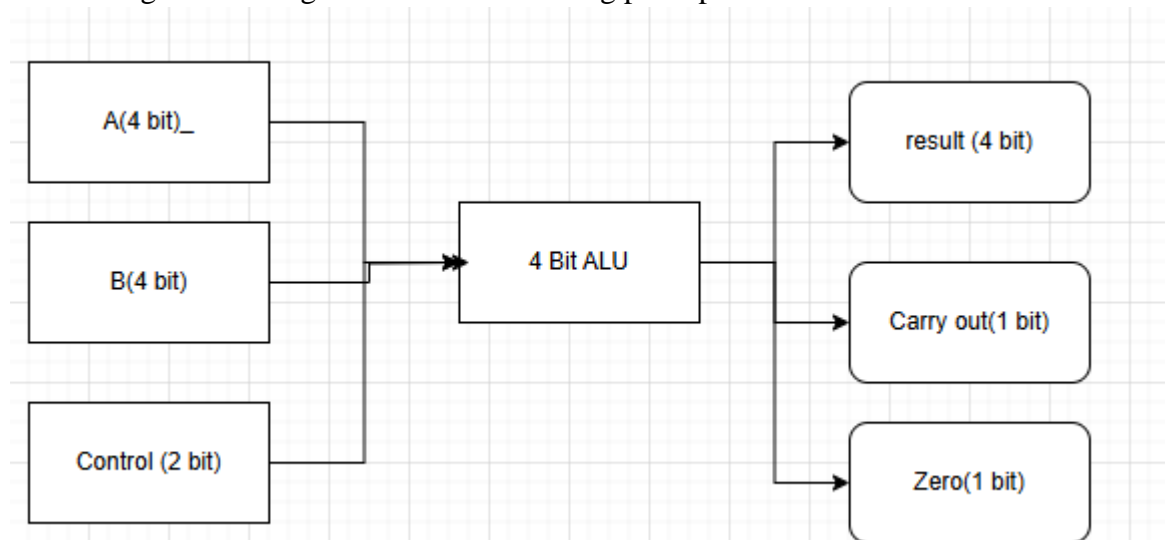
### 2) Block Diagram of designed ALU with working principle



The 4-bit ALU operates synchronously with the clock signal and performs one of four operations based on a 2-bit control input. When the control is 00, it adds inputs A and B, outputs the result, and sets the carry and zero flags accordingly. For 01, it subtracts B from A, with the result, carry (as borrow), and zero flag updated. When the control is 10, the ALU performs a Serial-In Serial-Out (SISO) left shift on input A, storing it in a shift register that shifts one bit left on each clock cycle; the shifted-out bit becomes the carry-out, and the zero flag reflects the current output. If the control is 11, a ring counter operation is executed by rotating the bits of A left, with no carry involved. In all cases, the ALU continuously updates the `result`, `carry_out`, and `zero` outputs on each positive clock edge based on the selected operation.

3) Logic Circuit for each block of the ALU with working principle (including Truth Table and Logic expressions)

- **4-bit Addition using full adders:**

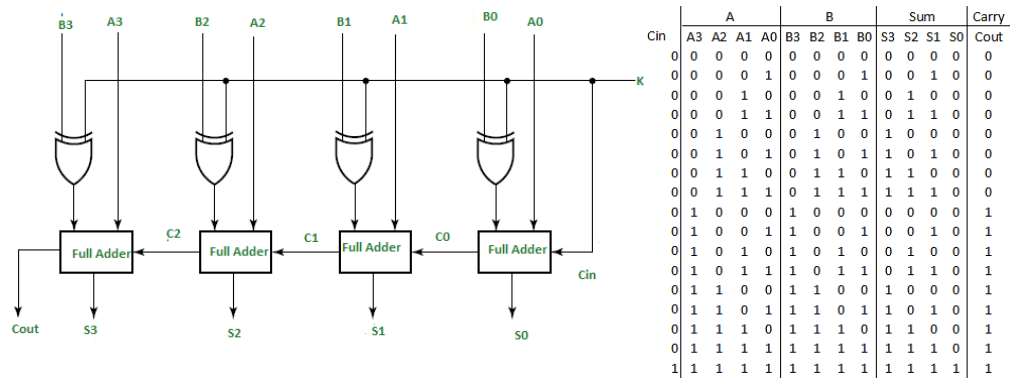


If Cin=0, it performs addition

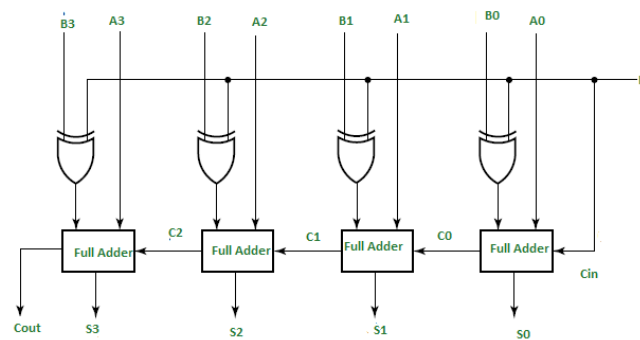**Logical expressions**

- $S = (A \oplus B) \oplus C_{in}$ : (XOR operation)
- $C_{out} = (A \cdot B) + (A \cdot C_{in}) + (B \cdot C_{in})$ : (AND and OR operations)

- **4-bit subtraction using full adders**




If Cin=1, it performs subtraction

**Logical expressions**

- $S_i = A_i \oplus B_i'' \oplus C_{i-1}$
- $C_i = (A_i \& B_i'') | (C_{i-1} \& (A_i \oplus B_i''))$

 - 4-bit left shift using SISO shift register




CLK	A0	A1	A2	A3
1st	1	0	1	0
2nd	0	1	0	0
3rd	1	0	0	0
4th	0	0	0	0

### Logical expressions

- $D_i = Q_{(i-1) \bmod N}$ , for  $i = 0, 1, 2, \dots, N - 1$

This gives the generalized form of the left shift for any  $N$ -bit SISO shift register.

- 4-bit Ring counter

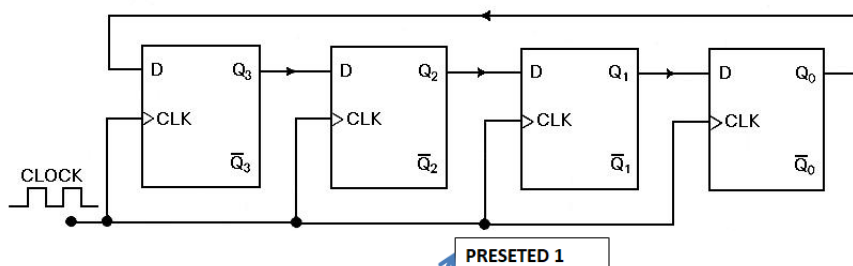

ORI	CLK	Q0	Q1	Q2	Q3
low	X	1	0	0	0
high	low	0	1	0	0
high	low	0	0	1	0
high	low	0	0	0	1
high	low	1	0	0	0

### Logical expressions

- $D_i = Q_{(i-1) \bmod N}$ , for  $i = 0, 1, 2, \dots, N - 1$

Where  $(i - 1) \bmod N$  represents the previous flip-flop in a cyclic manner.

## Verilog Code for Complete ALU Design and Sub-blocks of ALU:

```
module ALU (  
    input clk,          // Clock signal  
    input [3:0] A,       // 4-bit input A  
    input [3:0] B,       // 4-bit input B  
    input [1:0] control, // 2-bit control signal to select operation  
    output reg [3:0] result, // 4-bit result of operation  
    output reg carry_out, // Carry out for addition  
    output reg zero      // Zero flag  
);  
  
    reg [3:0] shift_reg; // Register for SISO left shift  
  
    always @(posedge clk) begin  
        case (control)  
            2'b00: begin // ADDITION  
                {carry_out, result} = A + B;  
                zero = (result == 4'b0000); // Zero flag  
            end  
  
            2'b01: begin // SUBTRACTION  
                {carry_out, result} = A - B;  
                zero = (result == 4'b0000); // Zero flag  
            end  
  
            2'b10: begin // SISO LEFT SHIFT  
                if (shift_reg == 4'b0000)  
                    shift_reg = A; // Initialize the shift register with input A  
                else  
                    shift_reg = {shift_reg[2:0], 1'b0}; // Shift left, shift in 0  
  
                result = shift_reg; // Update result with shifted value
```

```

        carry_out = shift_reg[3]; // MSB shifted out

        zero = (result == 4'b0000); // Zero flag
    end

    2'b11: begin // RING COUNTER

        result = {A[2:0], A[3]}; // Rotate bits to form a ring counter

        carry_out = 0;          // No carry in ring counter

        zero = (result == 4'b0000); // Zero flag
    end

    default: begin

        result = 4'b0000;

        carry_out = 0;

        zero = 1;

    end

endcase


end

endmodule

```

**Simulation Results** (Screenshots from the tool):

#### 4-bit Addition(8+4)

 

## 4-bit Subtraction(10-4)

Name	Value	3,338,409,899,990 ps	3,338,409,899,992 ps	3,338,409,899,994 ps	3,338,409,899,996 ps	3,338,409,899,998 ps
clk	1					
A[3:0]	a			a		
B[3:0]	4			4		
control[1:0]	1			1		
result[4:0]	06			06		
[4]	0					
[3]	0					
[2]	1					
[1]	1					
[0]	0					
carry_out	0					
zero	0					
shift_reg[3:0]	a			a		

## 4-bit Left Shift SISO shift register(A=10)

1<sup>st</sup> clock:


Name	Value	988,011,899,990 ps	988,011,899,992 ps	988,011,899,994 ps	988,011,899,996 ps	988,011,899,998 ps
clk	1					
A[3:0]	a			a		
B[3:0]	4			4		
control[1:0]	2			2		
result[4:0]	00			00		
carry_out	0					
zero	1					
shift_reg[3:0]	4			a		

2<sup>nd</sup> clock:


Name	Value	758,495,599,990 ps	758,495,599,992 ps	758,495,599,994 ps	758,495,599,996 ps	758,495,599,998 ps
clk	1					
A[3:0]	a			a		
B[3:0]	4			4		
control[1:0]	2			2		
result[4:0]	00			00		
carry_out	0					
zero	1					
shift_reg[3:0]	8			4		



3<sup>rd</sup> clock:

 

4-bit Ring Counter(A=10):

 


## Simulation Results


- Area (Utilization ) report:

### Summary

Resource	Utilization	Available	Utilization %
LUT	24	303600	0.01
FF	10	607200	0.00
IO	17	600	2.83

 

- **Power report:**

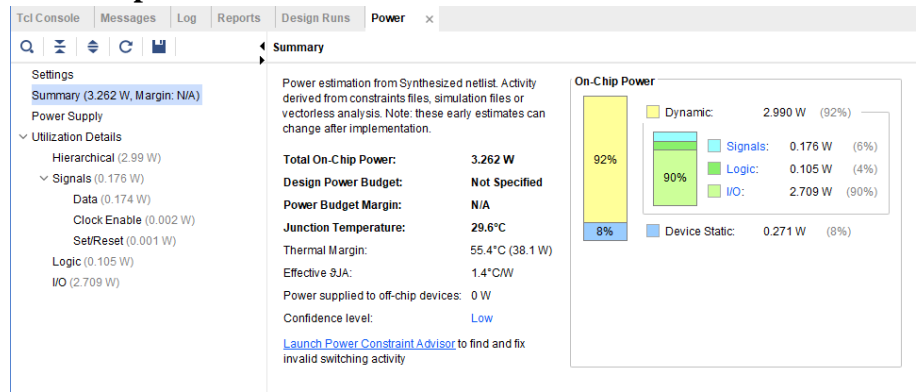

- **Timing report:**

Tcl Console Messages Log Reports Design Runs Timing x Power

Design Timing Summary

General Information

Timer Settings

Design Timing Summary

Check Timing (41)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 21	Total Number of Endpoints: 21	Total Number of Endpoints: NA

There are no user specified timing constraints.

## Conclusion:

The 4-bit ALU was successfully designed and implemented using Verilog to perform addition, subtraction, left shift (SISO), and ring counter operations based on a 2-bit control signal. The design correctly handled carry-out and zero detection, with all operations synchronized to the clock edge. Simulation results verified the correct functionality of each operation. The ALU design is efficient in terms of speed, area, and power, making it well-suited for FPGA implementation. Overall, the ALU meets the required functional and performance specifications effectively.